

LSI Circuit Design

**Behavior of MOS transistors Fundamentals
to LSI circuit design
Low power circuit technologies**

Author: Koichiro Ishibashi

Updated and reviewed by: Hai Pham

Renesas Design Vietnam Co., Ltd.


Contents

1. Introduction of Circuit Design
2. MOS transistor fundamentals
3. Fundamentals to LSI circuit design
4. Low power circuit technologies

Contents

1. Introduction of Circuit Design
2. MOS transistor fundamentals
3. Fundamentals to LSI circuit design
4. Low power circuit technologies

Chip Micrograph of SH4 Microprocessor

 

Technology 0.2 μ m
Tr. Count 3.3 M
Threshold Voltage 0.5V
Frequency 133-200 MHz
Power Supply 1.5-1.8V, 3.3V
Active Power 780 mW
Standby Current 100 μ A

**Designed in 1997
First SoC in Hitachi**

Location of Circuit Blocks in SH4


Cache Memories are kind of RAM that temporarily store instruction and data

PLL that generates clock signals


IO Circuits
that receive or send data

Logic Circuits

Data Path that executes calculation

 

Chip Micrograph of Mobile G4

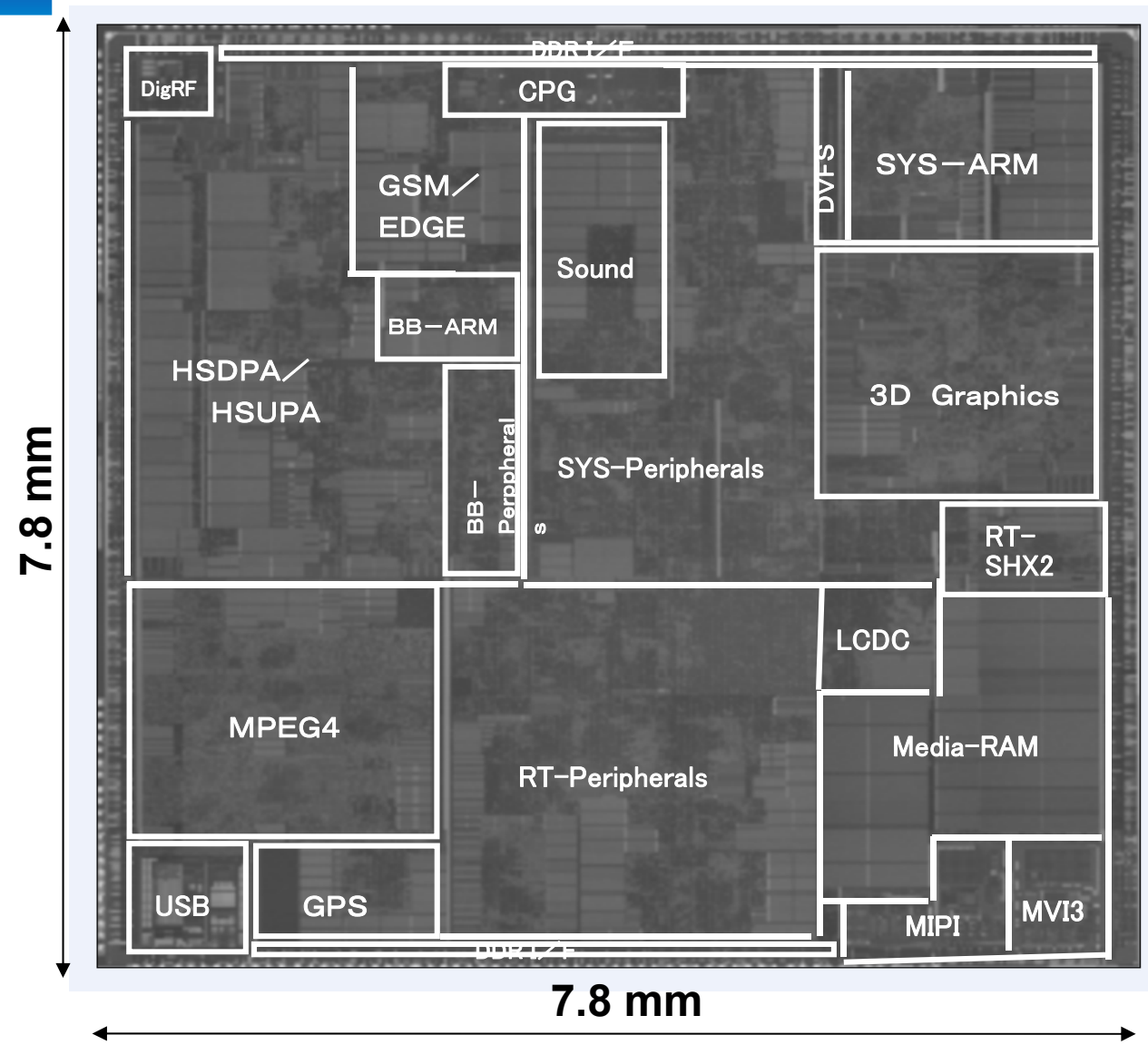


Technology	45 nm
Contents	45 M Gate 48.3M bit RAM 6.3Mbit ROM
Tr. Count	600M
CPU	
ARM A8	600 MHz
SHX2	400 MHz
Power Supply:	
Power domain	25
Core	1.15V – 1.0V (DVFS)
IO	LPDDR2 USB2.0
(DVFS: <i>Dynamic voltage-frequency scaling</i>)	

Designed by Renesas in 2009

SoC Design and Jigsaw Puzzle

 - **Jigsaw puzzle:** assemble whole picture from many of interlocking pieces
- **SoC design:** assemble whole chip from components in circuits libraries, place and route them, so that they function harmoniously



1. **Logic Cell library**
2. **Memory library**
3. **Analog Circuit library**

Circuit libraries on SoC

1. Logic cell library

- Primitive cells (Inverter, Buffer, NAND, NOR, FF, etc.)
- Data Path (Execution unit, selector, multiple-bit width)
- Clock Buffer
- Power Control Circuits (Power Switch, Substrate Bias Controller)

2. Memory library

- Register File
- RAM (Random Access Memory)
- ROM (Read Only Memory)

3. Analog Circuit library

- IO (Input and Output Buffer, Level Shifter)
- PLL (Phased Locked Loop)
- ADC (Analog to Digital Converter)
- RF (Radio Frequency Circuit)
- PA (Power Amplifier)


Note: Circuit blocks which indicated the red letters are implemented in SH4

Contents


1. Introduction of Circuit Design
2. MOS transistor fundamentals
 - 2.1 MOS structure
 - 2.2 NMOS operation
 - 2.3 PMOS operation
3. Fundamentals to LSI circuit design
4. Low power circuit technologies

NMOS FET Structure

<Cross Section view>

 


<Bird eyes view>

 


MOS: Metal-Oxide Semiconductor
STI: Shallow Trench Isolation

NMOS and PMOS FET Cross Section

PMOS FET

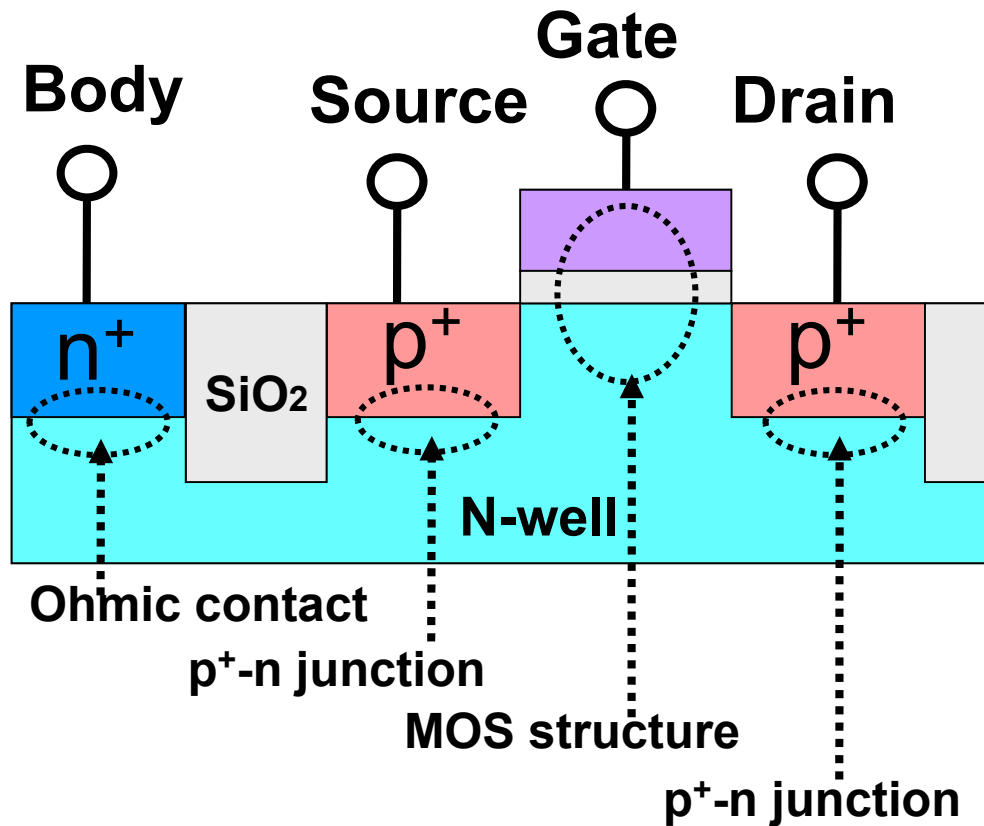


NMOS FET






 


MOS : Metal-Oxide Semiconductor
STI : Shallow Trench Isolation

Structure of CMOS

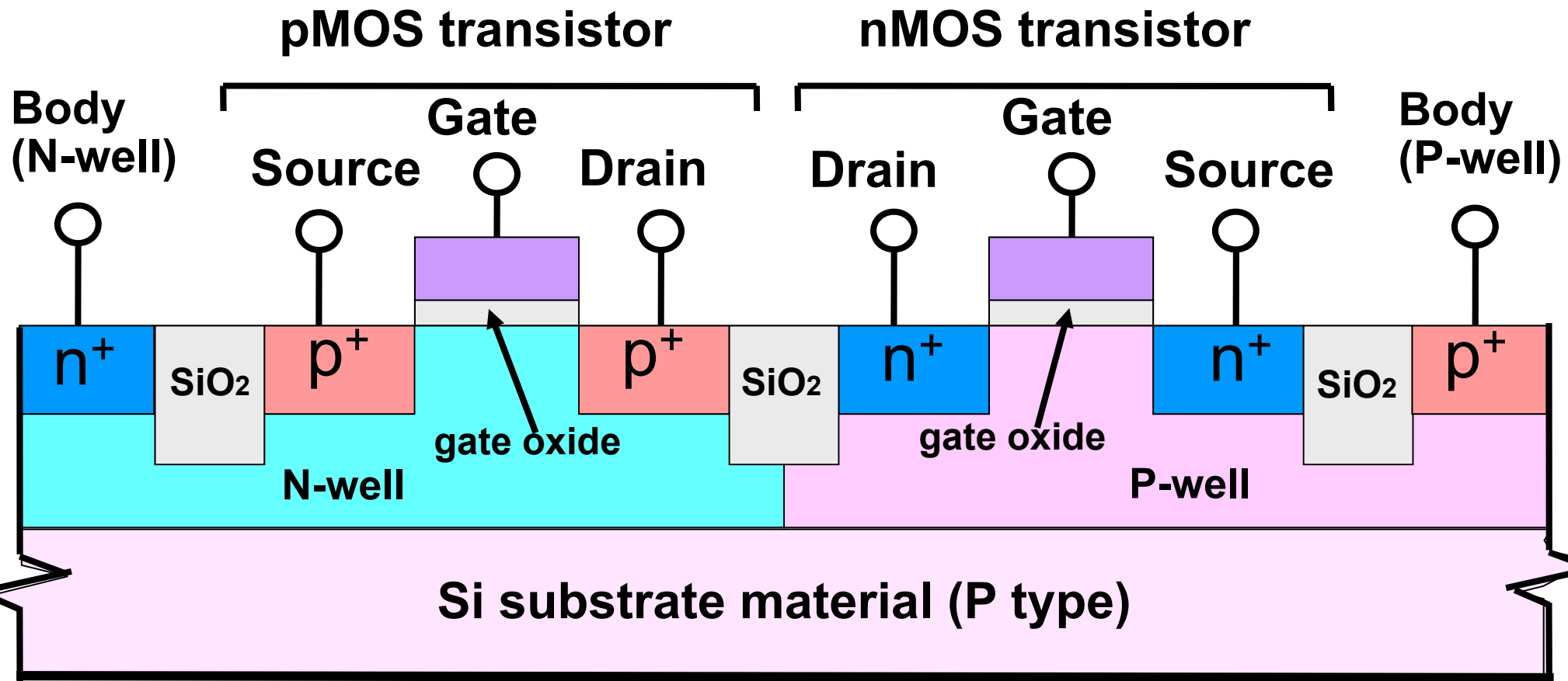


Notations and Operations of MOS Transistors

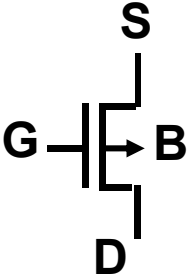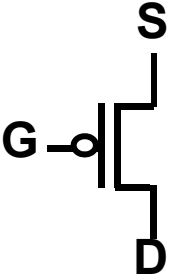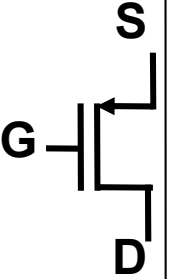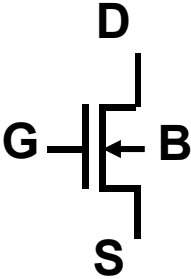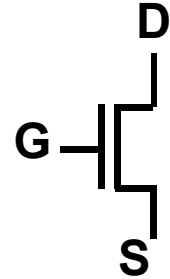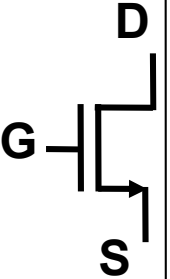	Notations			Operations
pMOS transistor				When <u>negative</u> gate voltage (V_{gs}) is applied, Holes are injected from Source and reach to Drain.
nMOS transistor				When <u>positive</u> gate voltage (V_{gs}) is applied, Electrons are injected from Source and reach to Drain.

All three notations are commonly used.


Naming Convention of MOS Transistor

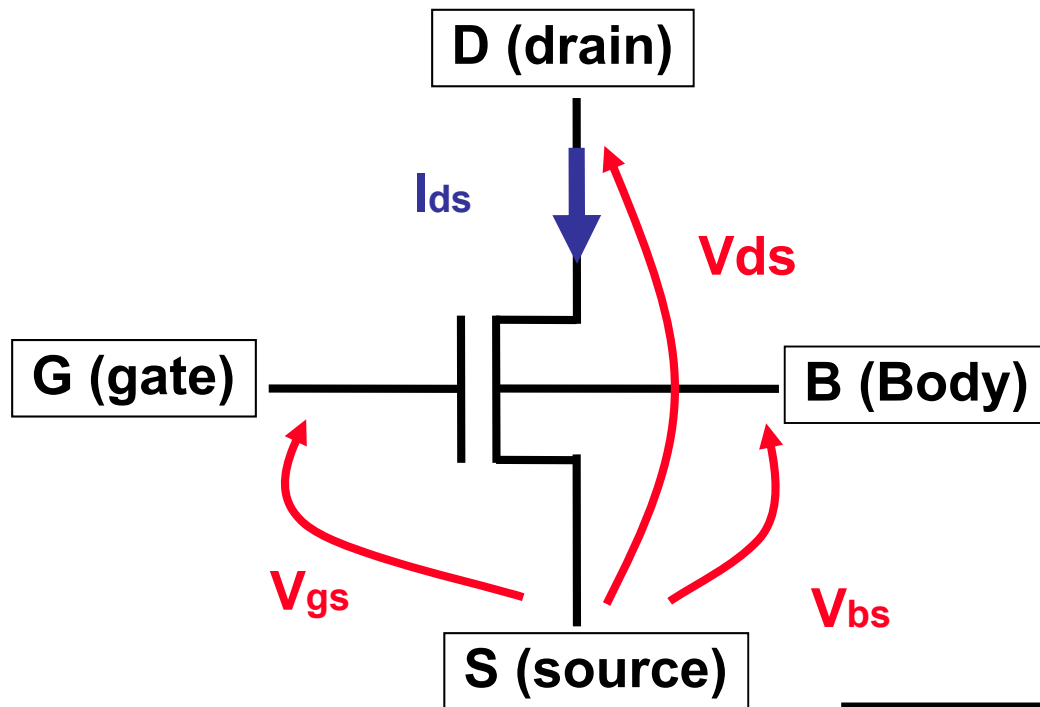

Sometimes “s” is eliminated, such as V_g , V_d , I_d , and V_b .

	Polarity			
	V_{gs}	V_{ds}	I_{ds}	V_{bs}
nMOS	+	+	+	-
pMOS	-	-	-	+

Operations of NMOS Transistor

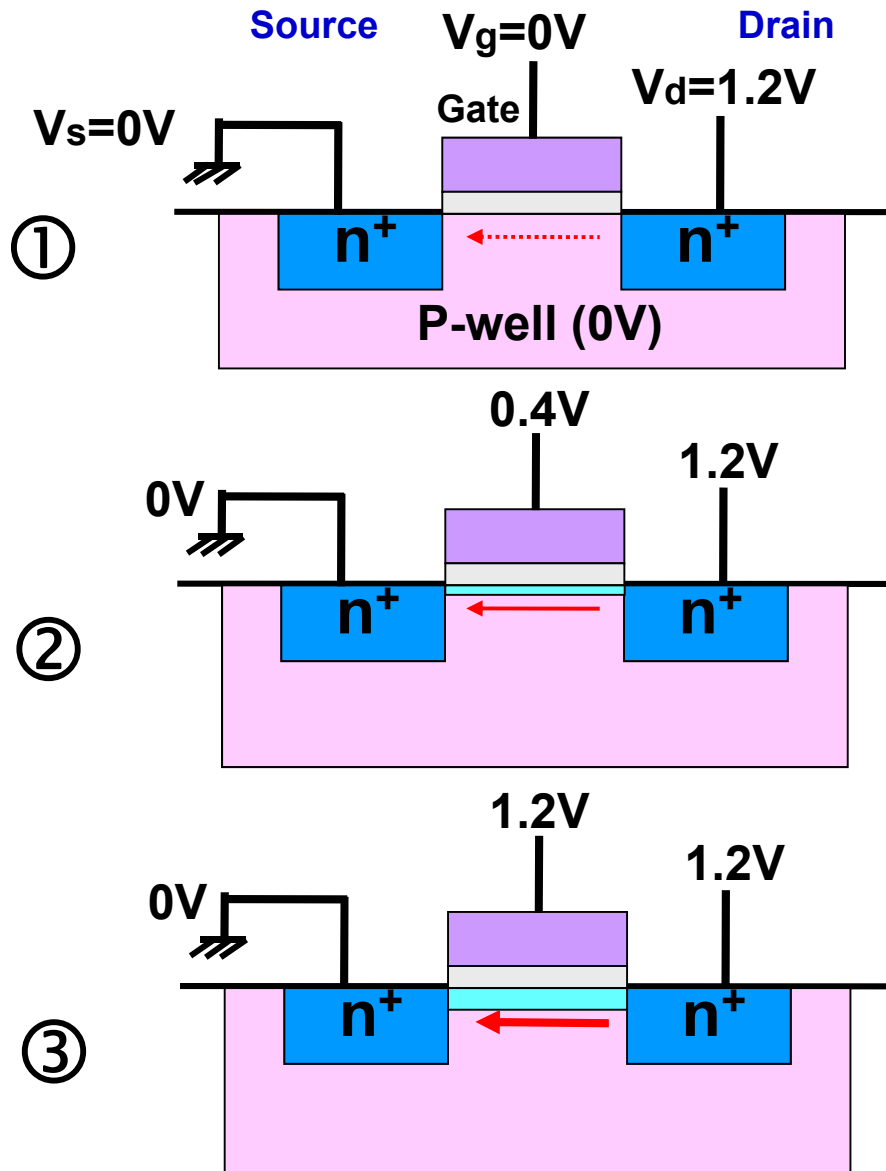

<Characteristics of drain current >

Only leakage current flows

Electrons are generated in the channel and current starts flowing

Number of electrons in the channel increases and current increases

Operations of NMOS Transistor

<Fundamental Formula of drain current>

$$I_d = \begin{cases} \beta_n \{V_d(V_g - V_{thn}) - V_d^2/2\} & \text{(Linear region)} \\ \beta_n/2 (V_g - V_{thn})^2 & \text{(Saturation region)} \end{cases}$$

$0 \leq V_d \leq V_g - V_{thn}$

$V_d > V_g - V_{thn}$

$\beta_n = \mu C_{ox} W/L$

μ : Electron Mobility


C_{ox} : Gate capacitance per unit area

W : Gate width

L : Gate length

V_{thn} : Threshold voltage of NMOS
(gate voltage required to switch ON transistor)

<Characteristics of drain current >

 



Drain current at $V_g = V_d = V_{dd}$ is called as **Saturation Conditions:**

$$V_{gs} - V_{th} > 0$$



$$V_{ds} > V_{gs} - V_{th}$$

Transistor acts as a two-terminal element depending on gate voltage



<Characteristics of drain current >

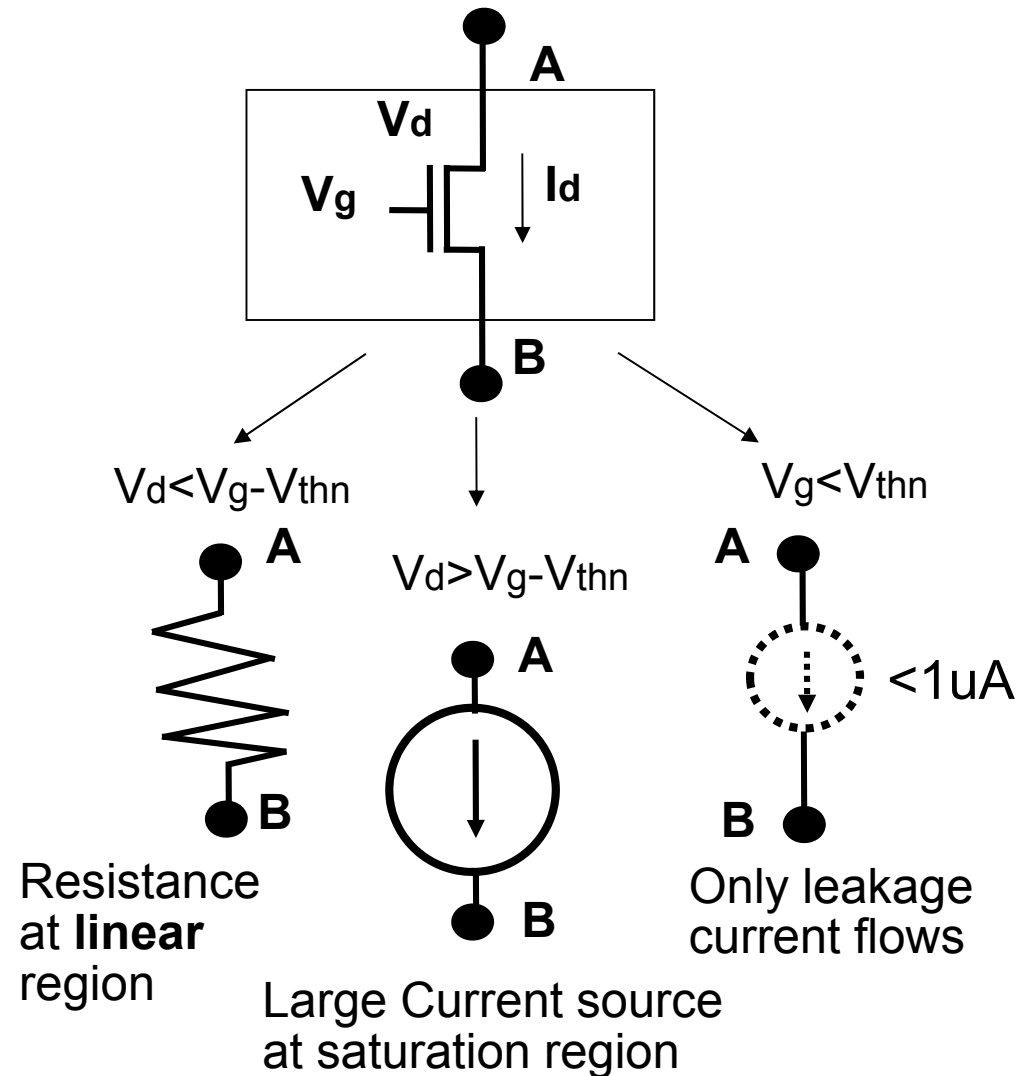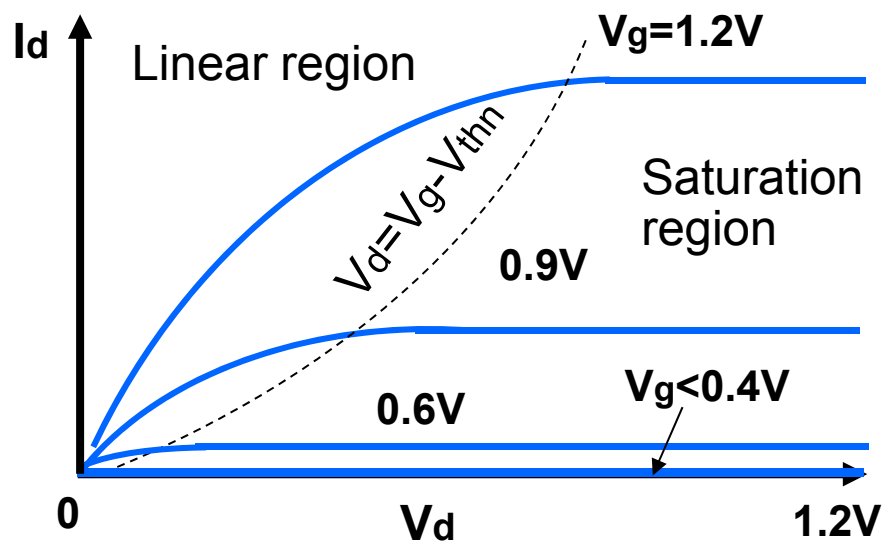


Threshold Voltage of NMOS (V_{thn})

  


<Characteristics of drain current>

  

Operations of PMOS Transistor

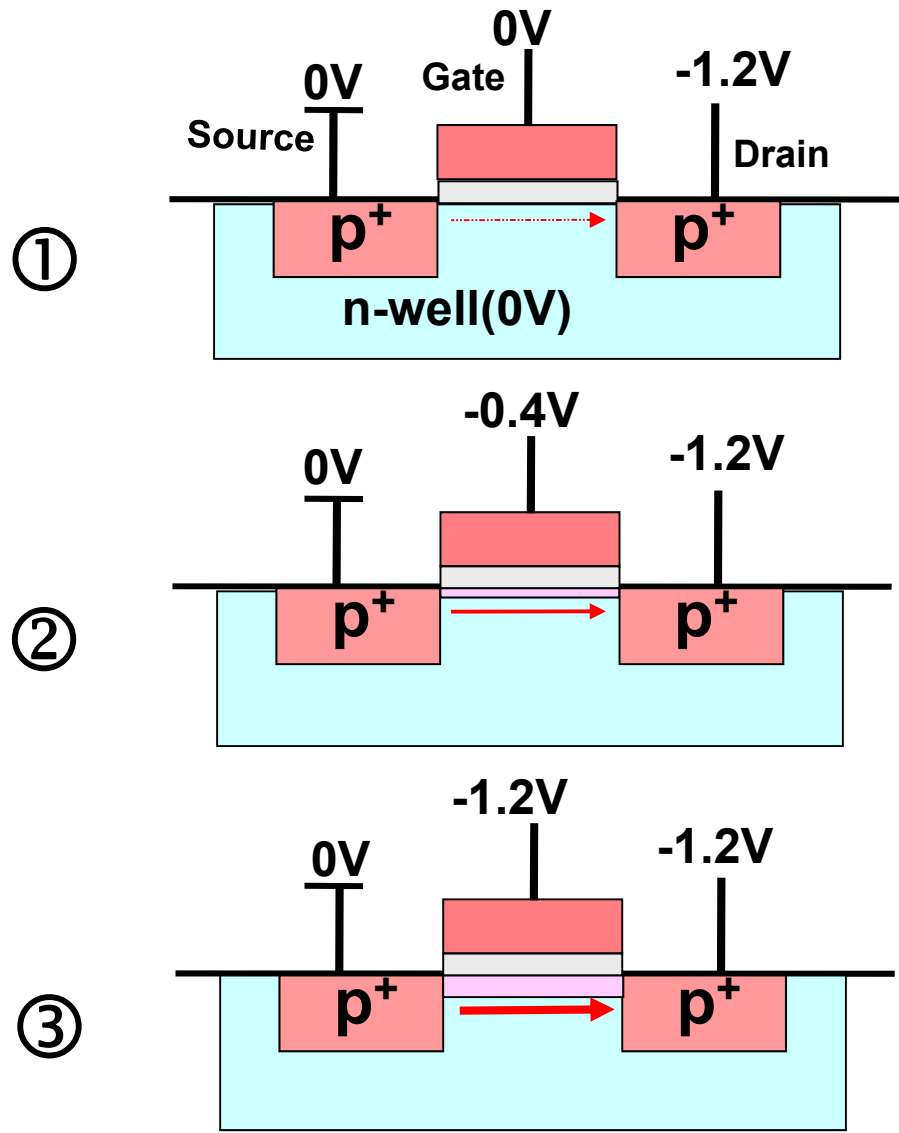

<Characteristics of drain current >

 

① Only leakage flows

② When holes are generated in the channel and current starts flowing


③ Number of holes increases and current increases

Question 1

Current flows from drain to source for NMOS, while it flows from source to drain for PMOS.

Why are the directions of currents different between NMOS and PMOS?


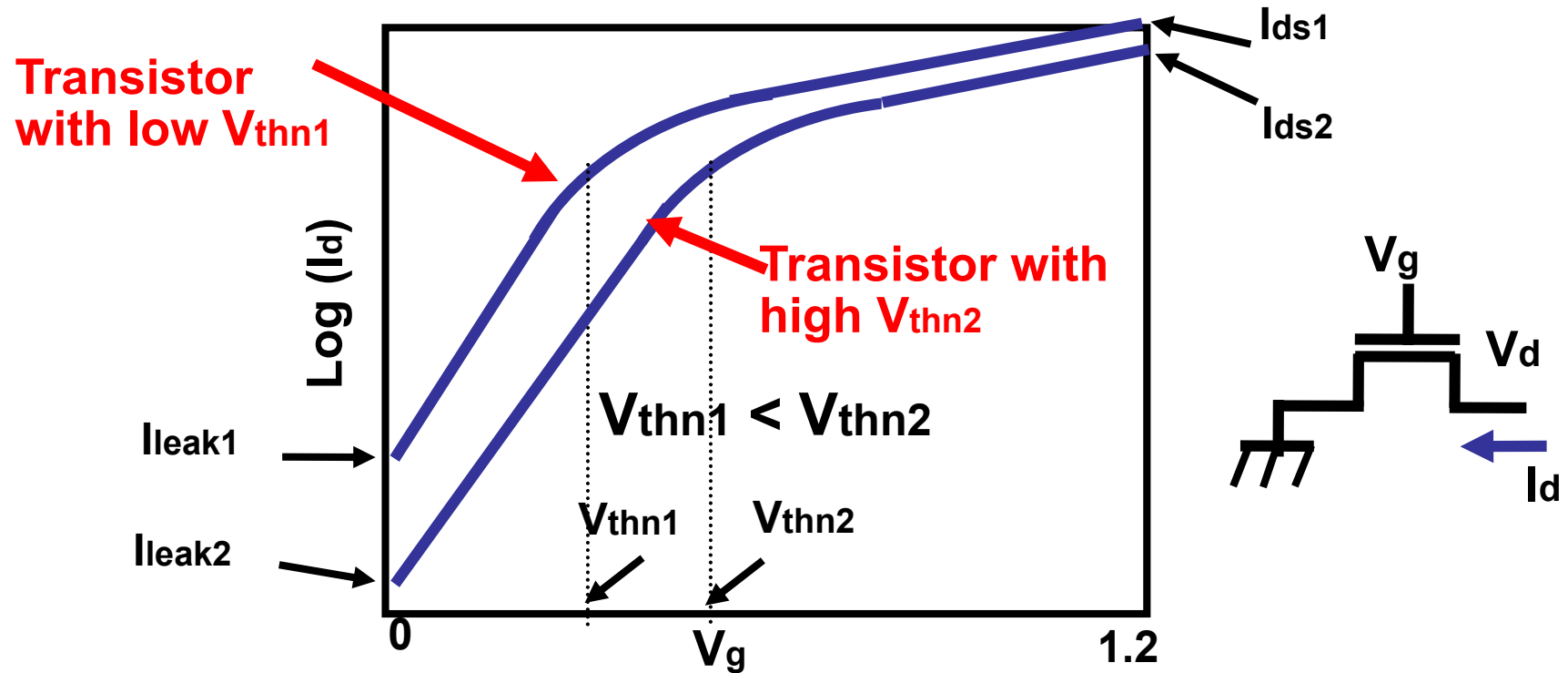
Threshold Voltage affects I_d and Leakage



- V_{th} can be tuned during fabrication by ion implantation.
- Transistor with lower V_{th} can flow large drain current at $V_g = 1.2V$, but has large leakage at $V_g = 0V$ ($I_{leak1} > I_{leak2}$)

Substrate (Body) Node Potential

 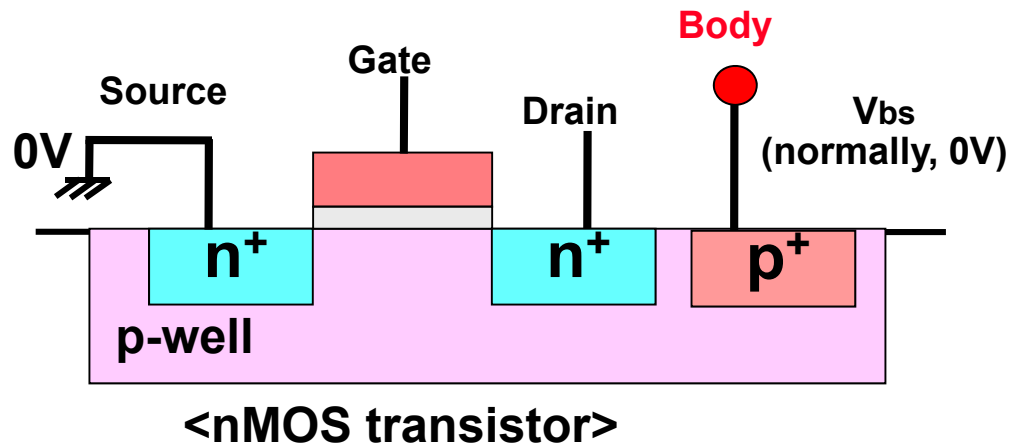- Electrical potential of body (formed by WELL structure) as 4th electrode also affects transistor characteristics.



< threshold voltage dependency on body voltage >

$$V_{thn} = V_{t0} + k^*(\sqrt{-V_{bs} + 2\phi} - \sqrt{2\phi})$$

V_{t0} , k , ϕ : constants

Body Effect

<nMOS>

- $V_{bs} \ll 0$, then V_{thn} increases.
- low speed, low leakage

<pMOS>

- $V_{bs} \gg 0$, then $|V_{thp}|$ increases.
- low speed, low leakage

Summary of MOS Transistor


- Characteristics of nMOS and pMOS transistors are symmetrical, and polarity of signals is opposite.
- I_d/V_d curves are divided into linear and saturation regions, where their boundary is $V_d = V_g - V_{th}$.
- I_d/V_g curve is divided into normal and sub threshold regions, where boundary is $V_g = V_{th}$.
- V_{th} affects I_d and leakage current:
When V_{th} is low, I_d becomes large but leakage also becomes large.
- Body electrode acts as 4th terminal, and body voltage V_{bs} affects V_{th} .

Contents


1. Introduction of Circuit Design
2. MOS transistor fundamentals
3. Fundamentals to LSI circuit design
 - 3.1 Inverter
 - 3.2 Other cells
4. Low power circuit technologies

Inverter

< CMOS inverter Cross Section >

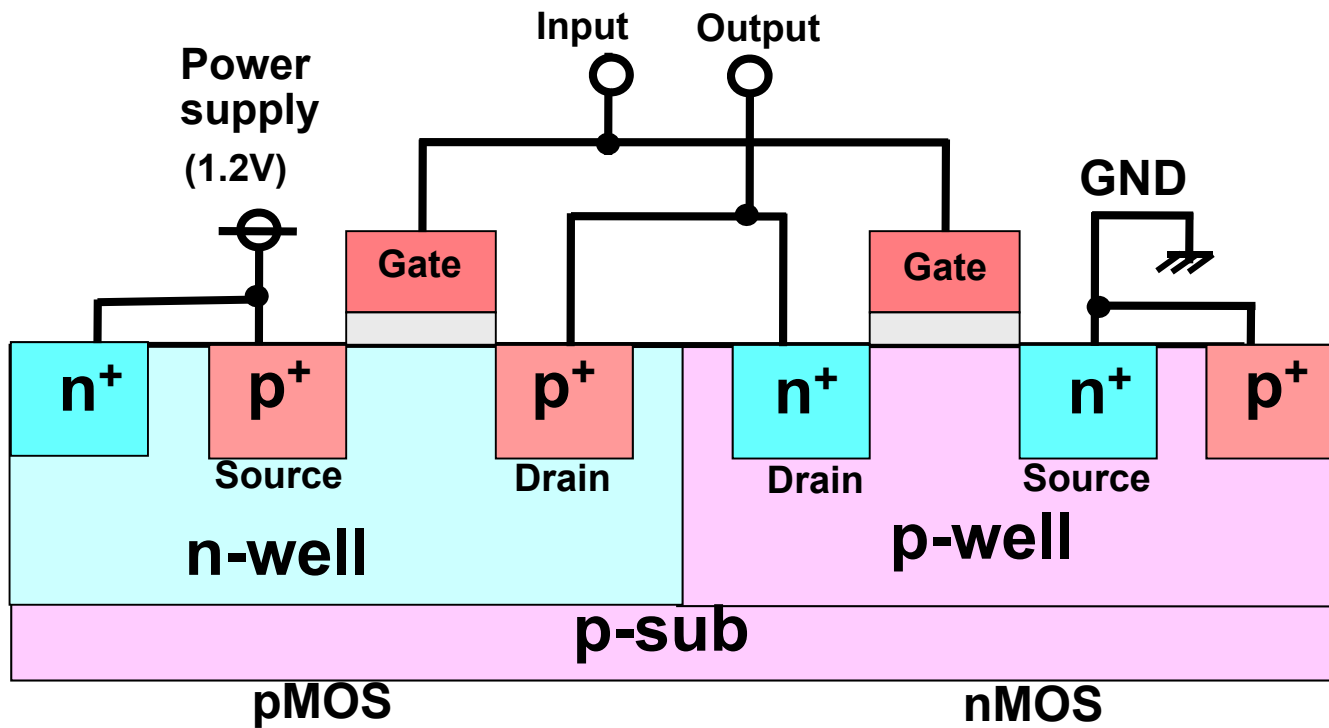


< Circuit Schematic >

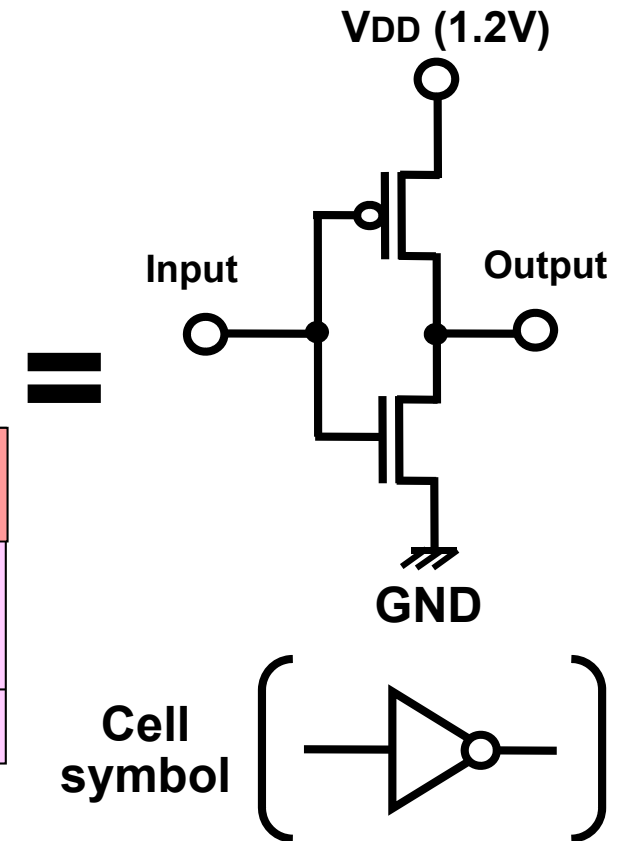


The most simple logic circuit with a pair of pMOS and nMOS transistors .

Inverter Design

<circuit schematics>

 

<Over View Layout>

 

INV Circuit Design: Define W and L of NMOS & PMOS depending on speed and drive-ability!


Wiring

1. Power lines


- Constant voltage lines
- Common to many transistors
- They prefer large capacitance to be stable
(Decoupling capacitance)

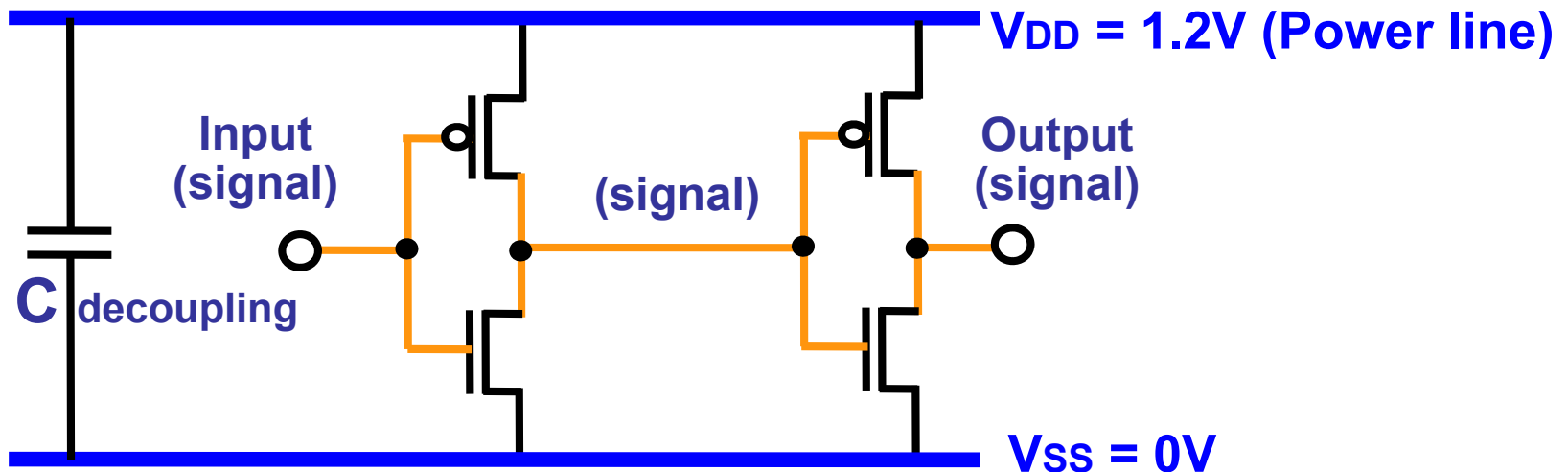2. Signal lines




- Wiring which transmits signals
- They prefer small parasitic capacitance to achieve short delay time



Logical Output Behavior

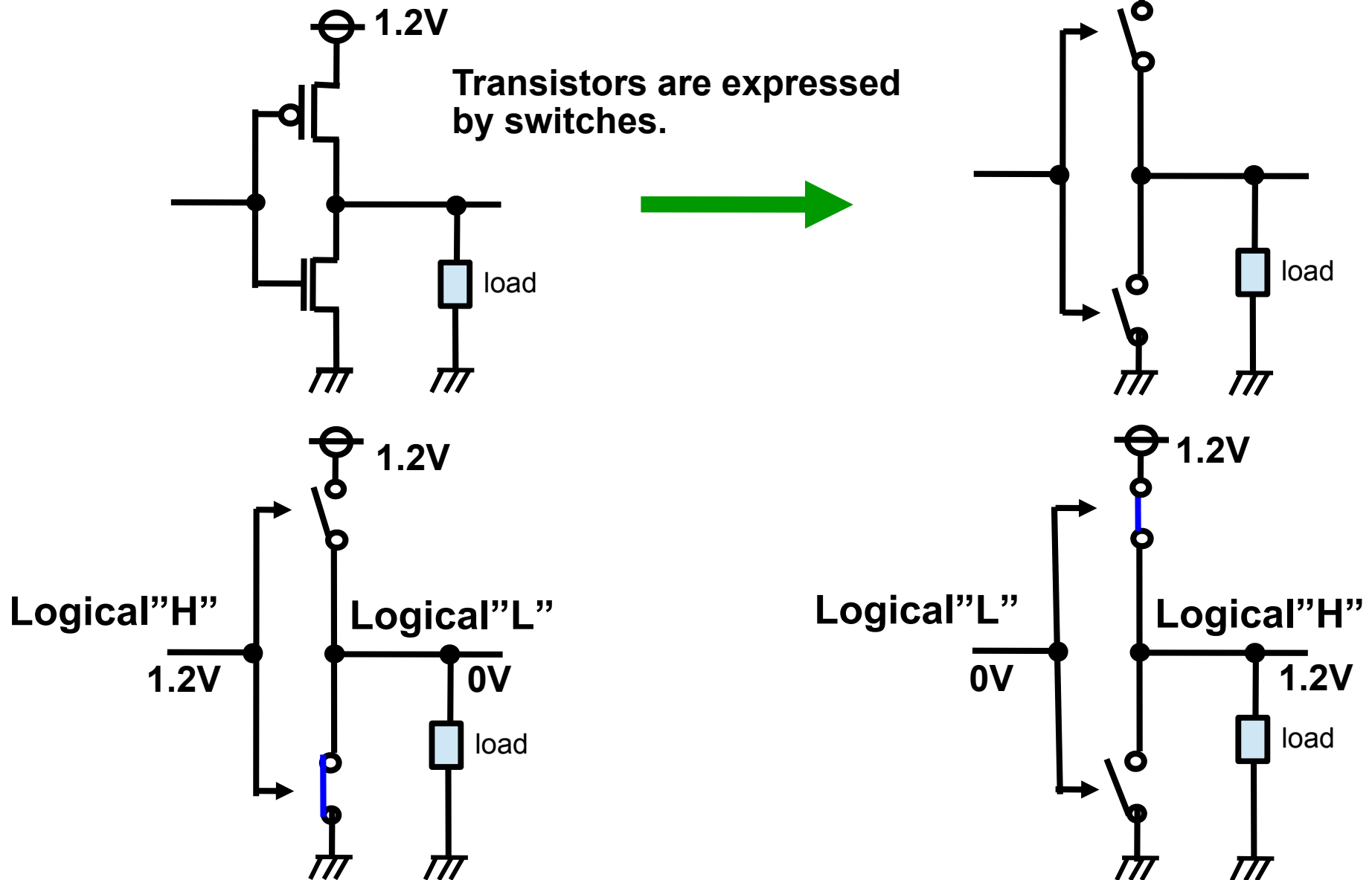



Drain Current Characteristics

   

Inverter performance is determined by saturation currents of both transistors.

Output voltage is determined by intersection point of NMOS & PMOS current curves.



Output Characteristics

 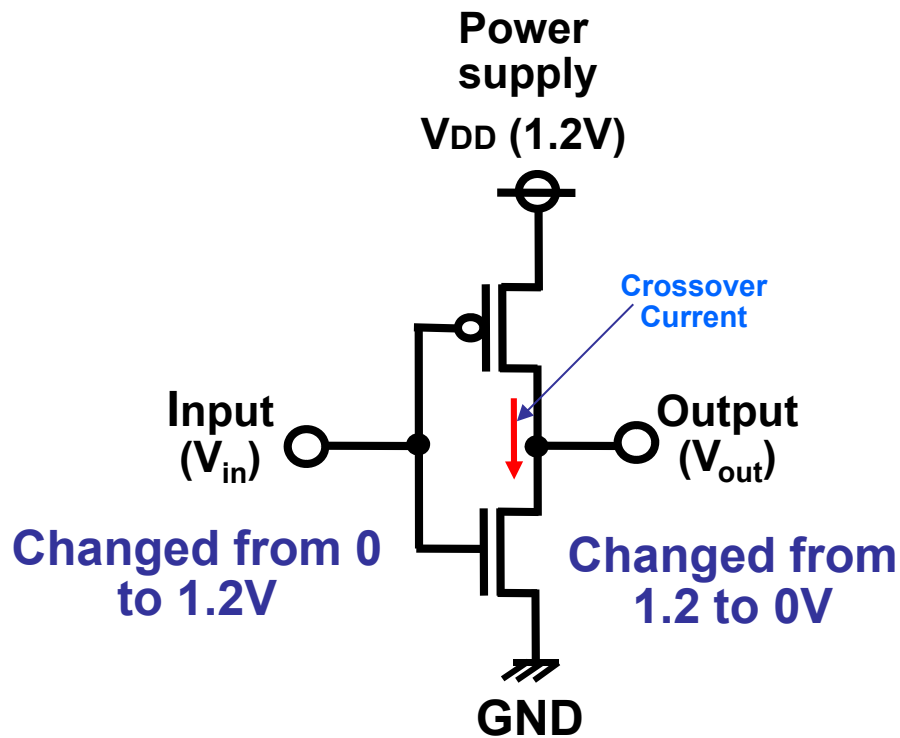

inverter: Signal at output is logically inverted from input

Neither NMOS or PMOS is ON (in steady state), no direct current flows;
No crossover current flows at stable states;

Logical Threshold Voltage

 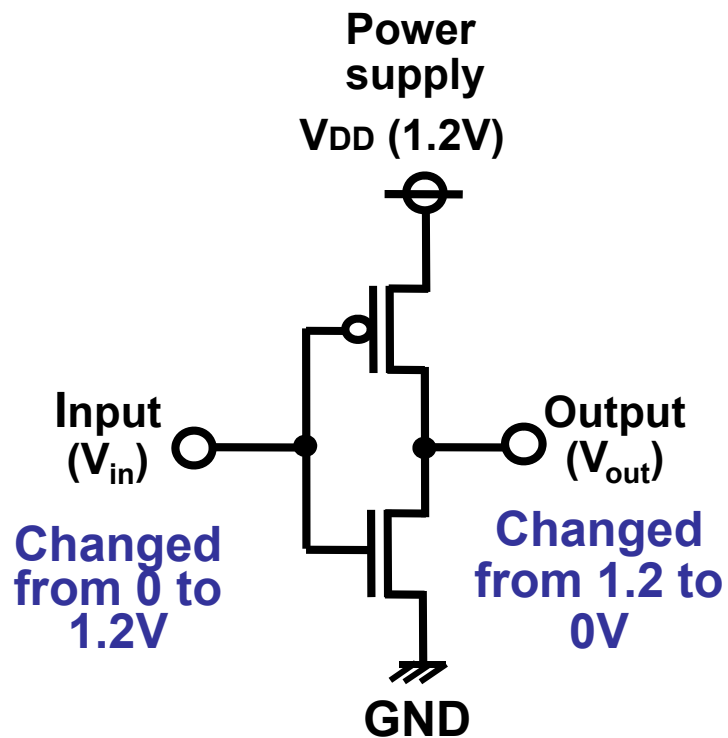


At V_{LT} , logic level is divided between "H" and "L". To set logical threshold voltage of each gate at the same level is important to secure noise margin:
 $V_{LT} = V_{DD}/2$;

Delay Definitions

Logic delay through a gate is conveniently described by the propagation delay time, t_p . This is average time needed for the output to respond to a change in the input logic state:

$$t_p = \frac{1}{2} (t_{pHL} + t_{pLH})$$



- **Falling propagation delay** (t_{pHL}):
Time for output to fall by 50% of V_{DD} references to input changes by 50% of V_{DD} ;
- **Rising propagation delay** (t_{pLH}):
Time for output to rise by 50% of V_{DD} references to input changes by 50% of V_{DD} ;
- **Fall time** (t_f):
Time for output to fall from logical level "1" to level "0";
- **Rise time** (t_r):
Time for output to rise from logical level "0" to level "1";

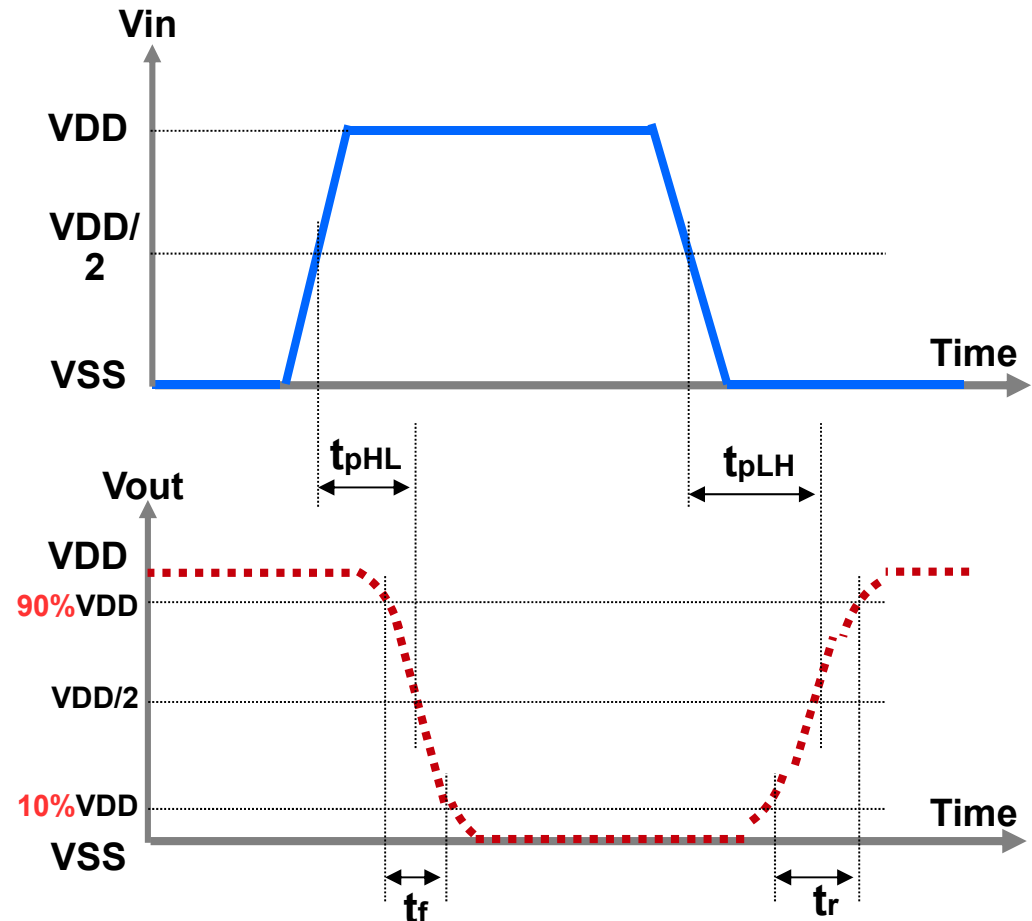

Logical level:


- Level "0": From V_{SS} to 10% of V_{DD} ;
- Level "1": From 90% of V_{DD} to V_{DD} ;

Charge up and Discharge

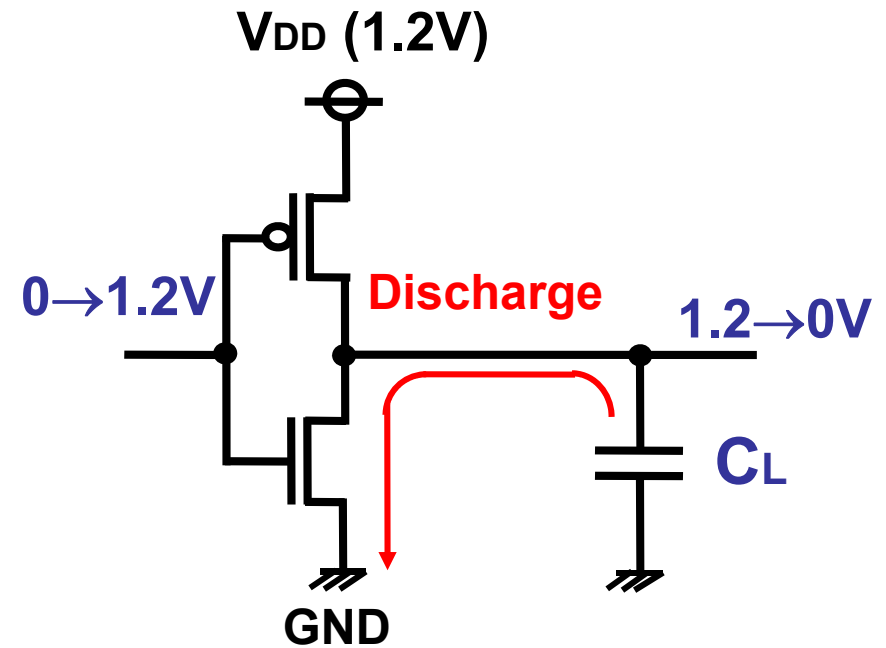 

Rise time and fall time: Times required to charge or discharge the load capacitor. Large load capacitance results in large delay.

Rise time - Delay for Charge up

 

Note: Assume at initial state, C_L was fully dis-charged to 0V!

- ◆ Current flows when pMOS is ON,

$$I_s = |I_{ds}| \\ = (\beta_p/2) \cdot (V_{DD} - |V_{thp}|)^2$$

- ◆ Electric charge to be charged

$$Q = C_L \cdot V_{DD}$$




Rise time is:

$$t_r = Q/|I_{ds}|$$

$$= \frac{C_L \cdot V_{DD}}{(\beta_p/2) \cdot (V_{DD} - |V_{thp}|)^2}$$

Fall time - Delay for Discharge

 

Note: Assume at initial state, C_L was fully charged to V_{DD} !

◆ Current flows when nMOS is ON,

$$I_{ds} = (\beta_n/2) \cdot (V_{DD} - V_{thn})^2$$

◆ Electric charge to be discharged

$$Q = C_L \cdot V_{DD}$$



Fall time is:

$$t_f = Q/I_{ds}$$

$$= \frac{C_L \cdot V_{DD}}{(\beta_n/2) \cdot (V_{DD} - V_{thn})^2}$$

Summary of Delay Time

$$\text{Delay time} = \begin{cases} \frac{C_L \cdot V_{DD}}{(\beta_p/2) \cdot (V_{DD} - |V_{thp}|)^2} & \text{: rise time} \\ \frac{C_L \cdot V_{DD}}{(\beta_n/2) \cdot (V_{DD} - V_{thn})^2} & \text{: fall time} \end{cases}$$

$$\beta = \underbrace{\mu}_{\text{Mobility}} \cdot \underbrace{C_{ox}}_{\text{Capacity of gate oxide per unit area}} \cdot W/L \quad \Rightarrow \quad \begin{cases} \blacklozenge \text{ Faster, if gate length } L \text{ is shorter} \\ \blacklozenge \text{ Faster, if gate width } W \text{ is wider} \end{cases}$$



Question 2

What are the schemes to shorten delay time of the inverter?


Other Logic Gates

  Examples of logic gates



○ 2 input NAND ($O = \overline{A \cdot B}$)



○ 2 input NOR ($O = \overline{A + B}$)

 

  ○ Combinational gate ($O = A \cdot B \cdot \overline{C}$)





With complementary transistor configurations, all logic circuits can be implemented. Basically their complementary operations are similar to those of an inverter.

Body effect in Logic Gate

  Examples of logic gates

○ 2 input NAND ($O = \overline{A \cdot B}$)





V_{thn} of NMOS transistor MNA is increased because V_{bs} becomes negative at discharge operation.



→ Delay timing will be increased!

Various Circuit Elements

NMOS Transmission Gate

  

CMOS Transmission Gate

  

Operation principle: NMOS Transmission Gate

V_{in} is at logical “1” (V_{DD}), assume at the initial state ($t=0$), $V_{out} = 0V$. Then:

$V_{GS} = V_{DD} > V_{thn}$;

$V_{DS} = V_{DD} \geq V_{GS} - V_{thn}$;


→ NMOS operates in Saturation region;

C_L is charging → V_{out} is increasing;

Condition for NMOS is ON: $V_{GS} \geq V_{thn}$;

→ $V_{out} \leq V_{DD} - V_{thn}$

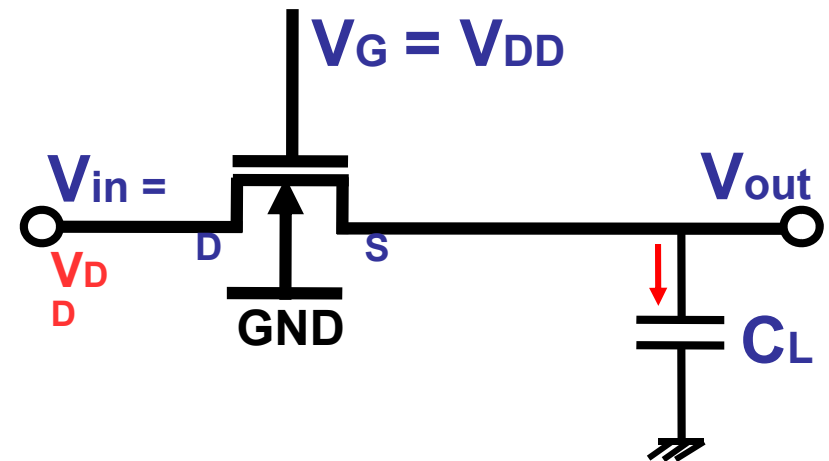→ V_{out} can only swing to $V_{DD} - V_{thn}$;



V_{in} is at logical “0” (0V), assume at the initial state ($t=0$), $V_{out} = V_{DD}$. Then:


$V_{GS} = V_{DD} > V_{thn}$; (always satisfied)

$V_{DS} = V_{DD}$; → NMOS is in Saturation region;

C_L is discharging → V_{out} is decreasing;

When $V_{DS} = V_{out} < V_{GS} - V_{thn}$, NMOS turns into Triode mode.

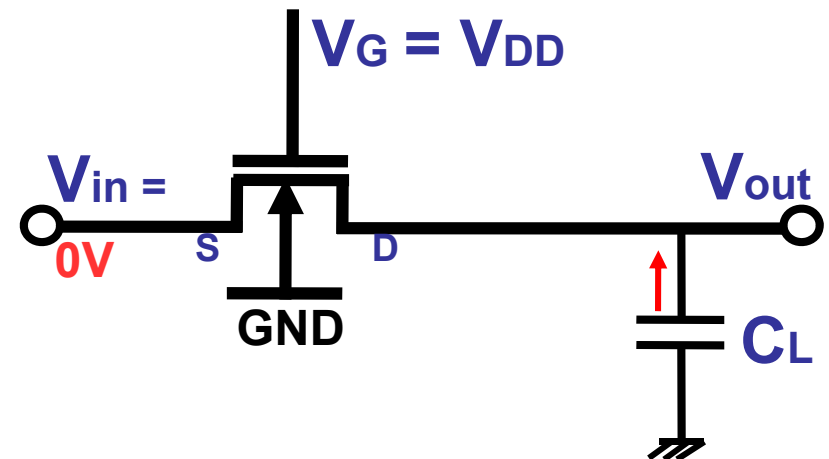C_L continues to discharge until $V_{out} = 0V$;



In case of disable mode ($V_G=0V$), output of NMOS Transmission gate becomes floating or high impedance.

Operation principle: CMOS Transmission Gate

V_{in} is at logical "1" (V_{DD}), assume at the initial state ($t=0$), $V_{out} = 0V$. Then:

- * For NMOS: $V_{GS} = V_{DD} > V_{thn}$; $V_{DS} \geq V_{GS} - V_{thn}$;
→ NMOS in Saturation mode;
- * For PMOS: $V_{SG} = V_{DD} > |V_{thp}|$; $V_{SD} \geq V_{SG} - |V_{thp}|$. → PMOS in Saturation mode;


C_L is charging → V_{out} is increasing;

- * PMOS is in SATURATION region only when:
(1) $V_{SG}(\text{PMOS}) \geq |V_{thp}|$ (always satisfy); and,
(2) $V_{SD}(\text{PMOS}) \geq V_{SG}(\text{PMOS}) - |V_{thp}|$
→ $V_{OUT} \leq |V_{thp}|$
→ At V_{out} is slightly greater than $|V_{thp}|$, PMOS turns to Triode region.

- * NMOS is ON when: $V_{GS}(\text{NMOS}) \geq V_{thn}$;
→ $V_{out} \leq V_{DD} - V_{thn}$

→ At V_{out} is slightly greater than $V_{DD} - V_{thn}$, NMOS turns to OFF state;

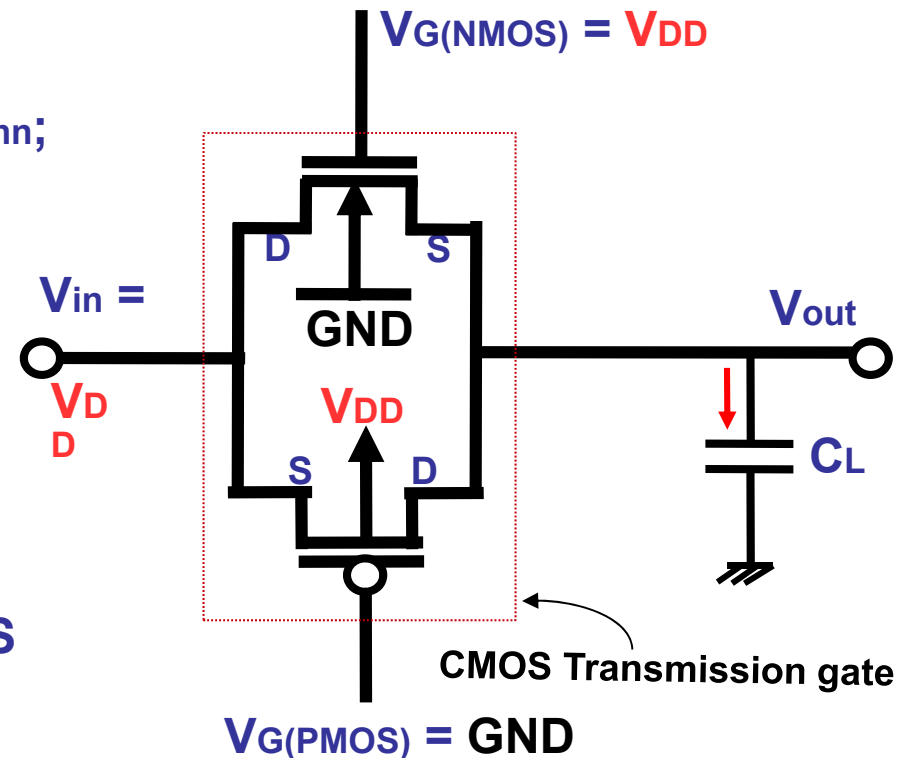But, PMOS is still in Triode region so, C_L continues to charge until $V_{out} = V_{DD}$.



Operation principle: CMOS Transmission Gate

V_{in} is at logical “0” (V_{ss}), assume at the initial state ($t=0$), $V_{out} = V_{DD}$. Then:

- * For NMOS: $V_{GS} = V_{DD} > V_{thn}$; $V_{DS} \geq V_{GS} - V_{thn}$;
→ NMOS in Saturation mode;
- * For PMOS: $V_{SG} = V_{DD} > |V_{thp}|$; $V_{SD} \geq V_{SG} - |V_{thp}|$. → PMOS in Saturation mode;


C_L is discharging → V_{out} is decreasing;

- * NMOS is in SATURATION region only when:
(1) $V_{GS(NMOS)} \geq V_{thn}$ (always satisfy); and,
(2) $V_{DS(NMOS)} \geq V_{GS(NMOS)} - V_{thn}$
→ $V_{out} \geq V_{DD} - V_{thn}$
→ At V_{out} is slightly lesser than $V_{DD} - V_{thn}$, NMOS turns to Triode region.

- * PMOS is ON when: $V_{SG(PMOS)} \geq |V_{thp}|$;
→ $V_{out} \geq |V_{thp}|$;
→ At V_{out} is slightly lesser than $|V_{thp}|$, PMOS turns to OFF state;


But, NMOS is still in Triode region so, C_L continues to dis-charge until $V_{out} = 0V$.

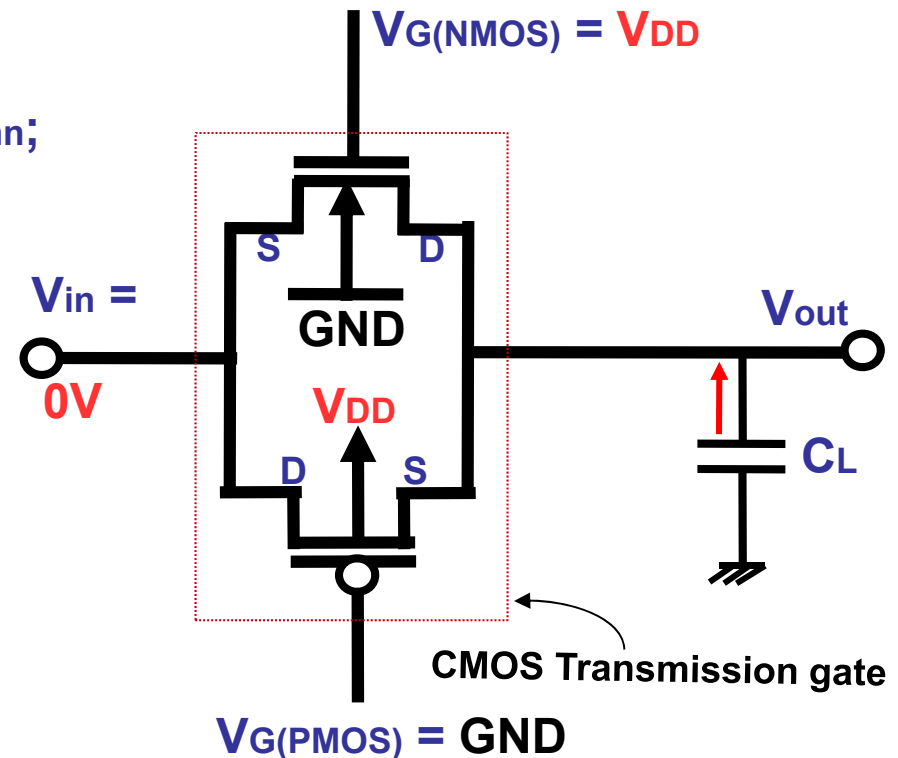In case of disable mode ($V_{G(NMOS)}=0V$, and $V_{G(PMOS)}=V_{DD}$), output of CMOS Transmission gate becomes floating or high impedance.




Summary Operation: CMOS Transmission Gate

 
Operation principle of CMOS Transmission gate can be summarized into two charts. First chart is for $V_{in}=V_{DD}$ where C_L is charging up; and other is for $V_{in}=0V$ where C_L is discharging.



 In case of disable mode $\phi=0V$, output of CMOS Transmission gate becomes floating or high impedance.






 $V_{in} = V_{DD}$; $C_L = 0V$ at initial state;





$V_{in} = 0V$; $C_L = V_{DD}$ at initial state;

Tri-state CMOS Inverter

  
 


Ring Oscillator

  

Connect odd number of inverter in ring configuration, the circuit oscillates.


Latch Circuit

  


Latch circuit can store data.

Various Latch Circuits


Tri-stage CMOS inverter type Latch

 


SR Latch Circuit

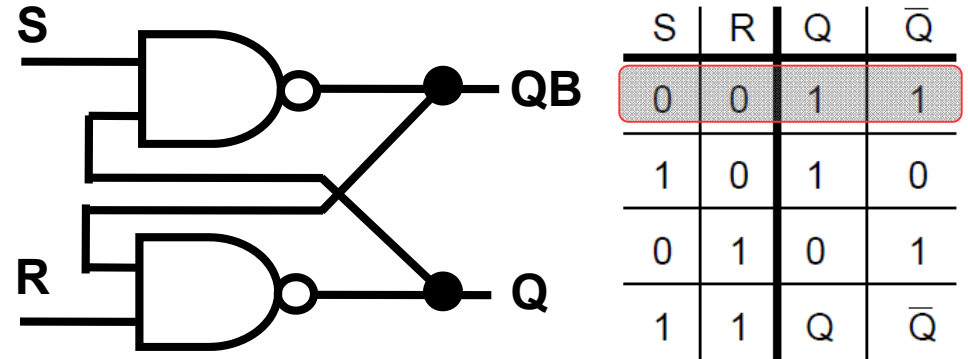


CMOS transmission gated type Latch

 

SRAM cell

 


Master Slave Flip Flop (FF) Circuit

 


Operation principle of FF


Principle of operation

 

 1. When ϕ becomes “Low” data “D” is taken into the first latch and the data “ \bar{D} ” appears at output of the first latch
2. When ϕ becomes “High” data “ \bar{D} ” is taken into the second latch and the data “D” appears at output of the second latch as a data of Q.



Setup and Hold Time of FF

 

(1) Data must be arrived to FF setup time before the clock edge.

(2) Data must be kept until hold time after the clock edge.

Setup and hold time is determined depend on FF circuit, and PVT conditions.

Question: What problem will happen if setup time, hold time are violated?

Metastability of FF (1/2)

What is metastability?

In picture, two bottom balls take up a stable state. They can leave only with the supply energy.



But the upper ball is different. Its state remains in unpredictable time and might fall down to unpredictable flank at unpredictable point of time by even very small and unknown influences.

State of this ball (upper ball) is metastable.

In FF, metastability means indecision of whether the output should be “0” or “1”.


How does FF enter metastability?

  When input D is rising (or falling) to V_{LT} , then ϕ become high. The value of \bar{D} might be this level (V_{LT}) for unpredictable periods. This is called metastability.




Metastability of FF (2/2)

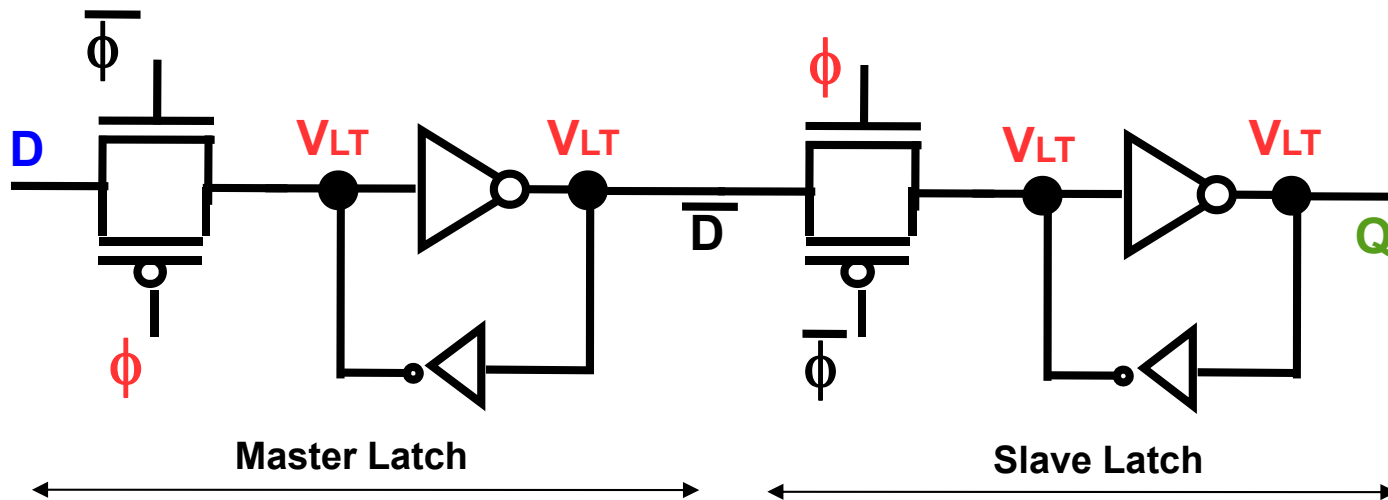How does FF output (FF/Q) response while FF is in metastability?



When Φ is rising (and assume that master latch is entering to metastability), slave latch is active. Then, value of \overline{D} is transferred to the inverter loop. So, the FF output (FF/ Q) will be also V_{LT} .

 FF/ Q will keep this potential level for unpredictable time and the final value is also unpredictable as shown on waveform picture.



Analog block: Operational amplifier (Op-amp)

An op-amp is a high gain voltage amplifier with differential inputs; and a single-ended output;

Circuit configuration:

- Biasing circuit: outlined in blue;
- Differential input stage: outlined in red;
- Output amplifier: outlined in green;



Bode plot:

Bode plot indicates frequency dependence of magnitude and phase;



- ω_1 , ω_2 : Frequency at pole1 and pole2 points;
- ω_u : Frequency at unity gain ($A_v=1$);
- ω_z : Frequency at zero point;

Applications of op-amp:

  - Voltage comparator;
- Schmitt Trigger; Triangle wave oscillator;
- Inverting/Non-inverting amplifiers;
- Differentiators and integrators; peak detectors;



Layout of Operational amplifier (Op-amp)

 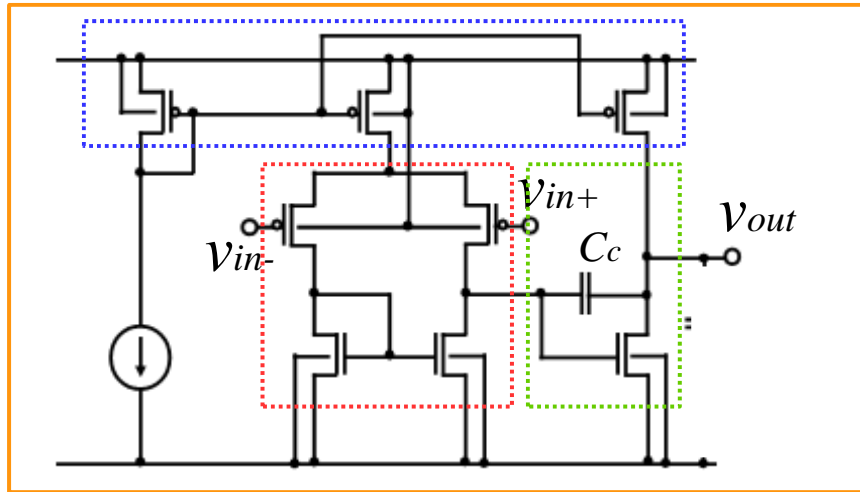


A sample layout of two-stage op-amp is designed in TSMC 40nm, size:

- width: 72.75 μm ;
- height: 43.61 μm ;


It is different compares to standard cell. Layout size of analog block does not have any standard, it depends on its position in whole placement of upper level.

It will be fabricated at whole chip level.

Block placement:

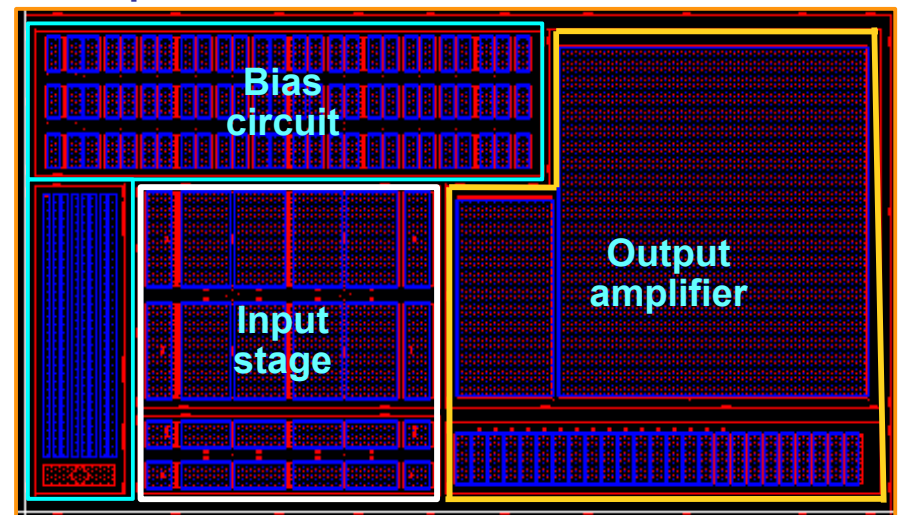


Standard Organization of Logic Block

 

Standard logic block is composed of combination logic sandwiched by 2 rows of FF

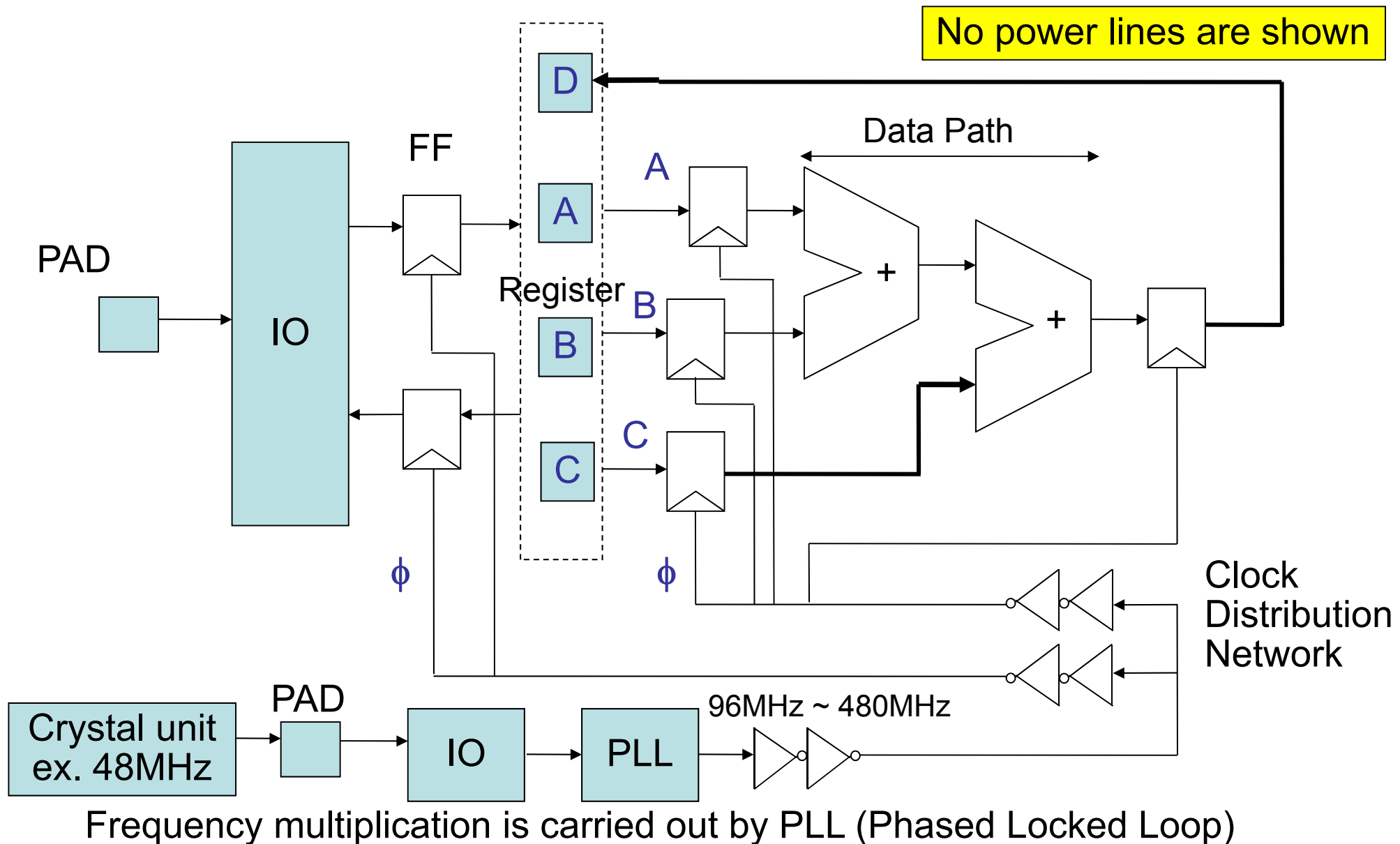
Basic Structure of SoC Synchronous Circuit



Summary for Logic Circuits

- Inverter, a fundamental logic circuit, is composed of a pair of nMOS and pMOS transistors, where both gates are commonly connected to input, and both drains to output.
- Output voltage is GND or V_{DD} , and no crossover current flows from V_{DD} to GND at stable conditions.
- Logical threshold voltage: $V_{LT} = V_{IN} = V_{OUT} \sim V_{DD}/2$
- Delay time:
$$T_d = \frac{C_L \cdot V_{DD}}{(\beta/2) \cdot (V_{DD} - V_{th})^2}$$
- Standard logic block is composed of combinational logic and FFs.

What Circuit Designers must do

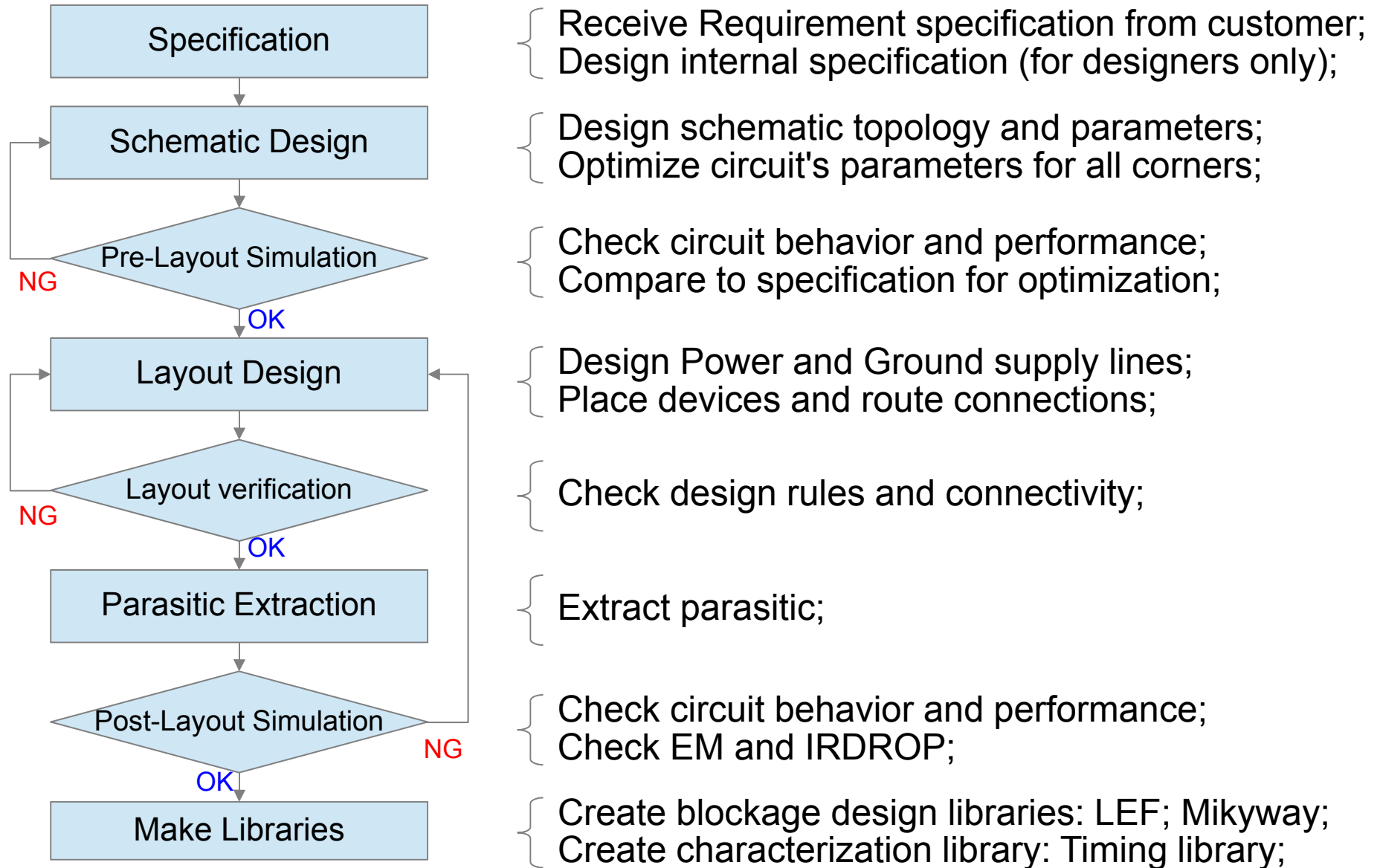

Thank you for your attention.



Renesas Design Vietnam Co., Ltd.

Confidential